


1.

- a) Below you can see on the left four binary numbers and on the right 4 interpretations of these numbers and a corresponding value. Match the number on the left to the descriptions on the right. (2 points)

| Binary Number | | Value, Interpretation | |
|---------------|-------|-----------------------|------------------------------------|
| 1 | 11110 | A | Decimal -1, 5-bit two's complement |
| 2 | 10001 | B | Decimal -1, 5 bit sign magnitude |
| 3 | 10010 | C | Decimal 30, 5 bit unsigned |
| 4 | 11111 | D | Hexadecimal 0x12, 5 bit unsigned |

1-C 2-B 3-D 4-A

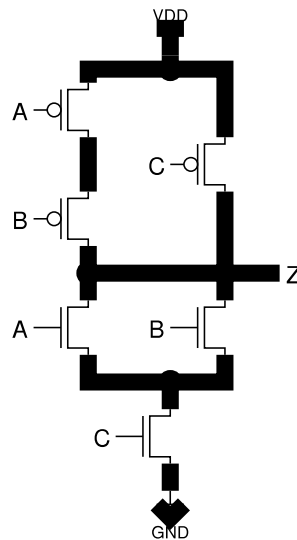- b) Consider the transistor level schematic below. What is the output going to be when A=1, B=0, C=1? (1 point)



0

- c) Using only 2-input AND, 2-input OR, or inverters, draw a gate level schematic that realizes the same Boolean Function as the circuit shown in 1(b). (2 points)

