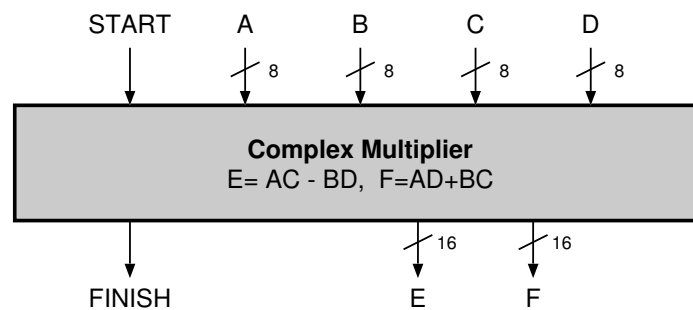



3. In this question we will investigate a circuit that can calculate the multiplication of two complex numbers expressed in the form $(a + bi)$ where a and b are integers expressed in 8-bit two's complement form and i is the complex number which satisfies the equation $i^2 = -1$. As you may remember the multiplication of two complex numbers is

$$\begin{aligned}(e + fi) &= (a + bi) \times (c + di) \\ &= (ac - bd) + (ad + bc)i\end{aligned}$$


The circuit that we will build has four separate 8-bit inputs (A, B, C, D) for the two complex numbers. A START signal is used to tell the circuit that a new pair of complex numbers are ready to be processed. The circuit has two 16-bit outputs (E, F) for the complex result, and a FINISH signal that tells that the circuit has result has been calculated and the result is ready at outputs E and F.



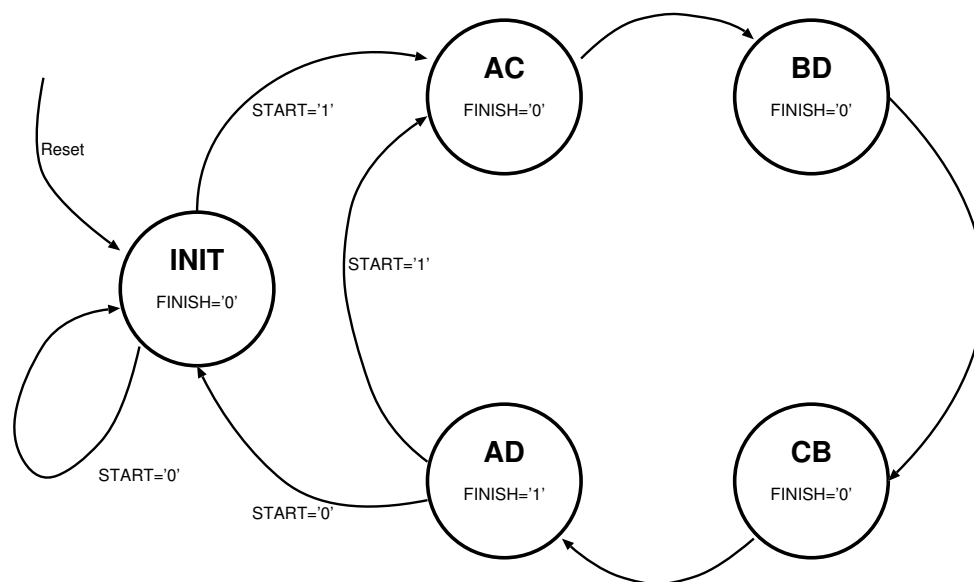A colleague of yours has designed an architecture that performs the complex multiplication operation serially using only one multiplier and an adder subtractor. The circuit is controlled by a finite state machine. The following is the state diagram of the state machine. The state names correspond to the operators used.



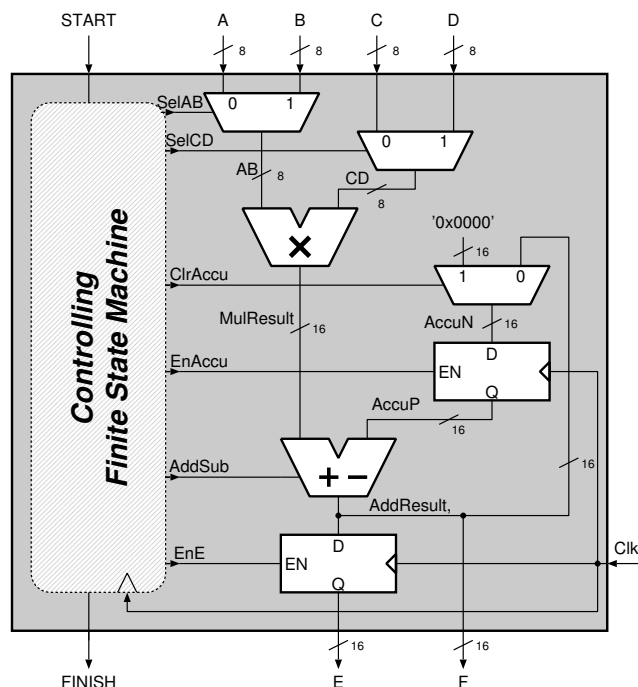The circuit block diagram is also given. It can be seen that the FSM controls a series of internal signals. We are interested in determining the correct value of these signals for each state.



- (a) (3 points) In your own words describe how the circuit works. For each of the calculation states (AC, BD, CB, AD), explain which operations take place:

When the Reset signal is active the circuit moves to the INIT state. The ClrAccu signal is '0' clearing the accumulator while in this state. The circuit stays in this state as long as START signal remains '0'...

Solution:

As soon as START is active, we first move to state AC. In this state, input A and C are selected and multiplied. The result goes to the accumulator. In the next state BD, this time inputs B and D are selected. This is subtracted from the accumulator, and the result is written to output register E. At the same time the accumulator is cleared. In the cycle CB, this time C and B are selected, multiplied and added to the accumulator. In the last cycle AD, inputs A and D are selected, multiplied and added to the accumulator. The output FINISH is set to 1. If the signal START is 1, the accumulator is cleared and the system moves to AC. Otherwise, the system moves to INIT state.

- (b) (7 points) Complete the following table, so that we can determine how to design the FSM.

Signal	Value	Description
SelAB	1	Select input B
SelCD	1	Select input D
ClrAccu	1	Assign the value '0' to the accumulator register input
EnAccu	1	Enable the accumulator register
AddSub	1	Perform Addition
EnE	1	Enable the register for output E

State	START	NextState	SelAB	SelCD	ClrAccu	EnAccu	AddSub	EnE	FINISH
INIT	0	INIT	X	X	1	1	X	0	0
INIT	1	AC	X	X	1	1	X	0	0
AC	X	BD	0	0	0	1	1	0	0
BD	X	CB	1	1	1	1	0	1	0
CB	X	AD	1	0	0	1	1	0	0
AD	0	INIT	0	1	1	1	1	0	1
AD	1	AC	0	1	1	1	1	0	1