

**Problem 1 (10 points)**

i.

ii. (2 points) Select which of the following always outputs 0

a.  $x^1$

b.  $x^x$

c.  $\sim(x^x)$

d.  $x^0$

iii.

**Problem 2 (10 points)**

What are the minimum required number of AND, OR gates required to implement F as a sum-of-products. Assume you have inputs and their complements available as inputs to your circuit.

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- a) One 2-input gate
- b) One 3-input gate
- c) Two 2-input gates
- d) Two 3-input gates
- e) One 2-input gate and one 3-input gate
- f) Three 2-input gates
- g) Three 3-input gates
- h) Two 2-input gates and one 3-input gate
- i) None of the above

### Problem 3 (10 points)

Let's use the subscript to denote the base number system. That is:  $(1011)_2$  implies binary representation, while  $(B)_{16}$  implies the same number in hexadecimal (base-16).

- i. (3 points) Select all the options which are strictly smaller than  $(136)_{10}$ 
  - a.  $(1000\ 0100)_2$
  - b.  $(89)_{16}$
  - c.  $(88)_{16}$
  - d.  $(1000\ 1000)_2$
  - e. None of the above
  
- ii. (5 Points) If all these values are encoded as two's complement, select the true statement:
  - a.  $C7 + BB = (7E)_{16}$
  - b.  $C7 + BB = (126)_{10}$
  - c.  $C7 + BB = (82)_{16}$
  - d. None of the above
  
- iii. (2 points) If these hexadecimal numbers represent two's complement encoded values, circle the largest value
  - a. C4
  - b. C6
  - c. E8
  - d. 70

**Problem 4 (10 points)**

(6 points) Each of the numbers below is represented in two's complement, each variable, w, x,y,z can be any hexadecimal value independently of each other.

i.

$$\begin{array}{r} (B3X1)_{16} \\ + (47WZ)_{16} \\ \hline \end{array}$$

- a) i. and ii. both can result in overflow
- b) i. can result in overflow, but not ii.
- c) i. cannot result in overflow but ii. can
- d) neither i. nor ii. can possibly result in an overflow

ii.

$$\begin{array}{r} (7YCD)_{16} \\ + (0110)_{16} \\ \hline \end{array}$$

(4 points) Consider integers  $X[15:0]$  and  $Y[15:0]$  that result in  $SUM[15:0]$  when added. If we know the values of  $X[15:14]$  and  $Y[15:14]$  as well as  $SUM[15]$  we can always determine if there's an overflow:

- a. For signed integers only, not for unsigned integers
- b. For both signed and unsigned integers
- c. For unsigned integers only not for signed integers
- d. We cannot **always** determine if there's been an overflow in either case

**Problem 5 (10 points)**

1. (3 points) If you had to make a 2:1 multiplexor (2 inputs, 1 select bit) using only NAND gates. How many NAND gates would you need?
  - a. 3
  - b. 4
  - c. 5
  - d. 6
  - e. 7
  - f. 8
  - g. None of the above
  
2. (3 points) If you had to make a 2:1 Decoder (2 outputs, 1 select bit) using only NOR gates. How many NOR gates would you need?
  - a. 3
  - b. 4
  - c. 5
  - d. 6
  - e. 7
  - f. 8
  - g. None of the above
  
3. (4 points) A Majority gate, with output  $f$  and inputs  $a$ ,  $b$ , and  $c$  is given by  $f = a \& b \mid a \& c \mid b \& c$ . If you could only use 2- and 3-input NAND gates, how many such gates would you need to implement this function?
  - a. 3
  - b. 4
  - c. 5
  - d. 6
  - e. 7
  - f. 8
  - g. None of the above

### Problem 6 (10 points)

- i. (2 points) Consider a two-input XOR gate with two inputs and one output. Given the ability to set the inputs to constants (e.g., 1/0). Is it possible to construct a NAND gate using an infinite supply of such two-input XOR gates?

a. Yes

b. No

- ii. (4 points) Given only NAND gates, what is the minimum number of NAND gates needed to implement a two-input XOR.

a. 3

b. 4

c. 5

d. 6

e. 7

f. 8

- iii. (4 points) Below is the Verilog code for two modules, thing and unknown:

```
module thing (  
    input  a,  
    input  b,  
    output y  
);
```

```
    assign y = a & ~b | b & ~a;
```

```
endmodule
```

```
module unknown (  
    input  a,  
    input  b,  
    input  c,
```

```

output y
);

wire w;


thing thing1 (
    .a (a),
    .b (b),
    .y (w)
);

thing thing2 (
    .a (w),
    .b (c),
    .y (y)
);


endmodule

```

 The following waveforms are applied to the inputs of unknown:



 Which of the following is the correct waveform for output y of module unknown?



- a.  $y_1$
- b.  $y_2$
- c.  $y_3$
- d.  $y_4$



**Problem 7 (10 points)**

i. (3 points) Given a Karnaugh map for a 4-input function, the maximum number of product terms that can ever remain after minimization are:

a. 6

b. 7

c. 8

d. 9

e. Impossible to determine without knowing the entries

ii. (3 points) Select all the correctly minimized expressions for the K-Map below

ab \ cd	00	01	11	10
00		1	1	1
01				
11				
10	1			1

a.  $(\sim a \& \sim b \& d) \mid (a \& \sim b \& \sim d) \mid (\sim a \& \sim b \& c)$

b.  $(\sim a \& \sim b \& \sim d) \mid (\sim a \& \sim b \& d) \mid (\sim b \& c \& \sim d)$

c.  $(\sim a \& \sim b \& d) \mid (a \& \sim b \& \sim d) \mid (\sim b \& c \& \sim d) \mid (\sim a \& \sim b \& c)$

d. none of the above



### Problem 9 (10 points)

A De-Multiplexor or a DEMUX takes an input (X) and places it on one of  $2^n$  outputs ( $Y[2^n-1:0]$ ) based on an n-bit selection input ( $S[n-1:0]$ ).

- i. (4 points) Partial verilog code is provided to correctly describe a DEMUX.

```
module demux(  
  input X,  
  input S,  
  output [1:0] Y  
);  
  
...  
  
endmodule
```

  - ii. The input to the DEMUX looks is provided below



Answer some questions about a testbench for the DEMUX.

- iii. (2 points) Select all the true statements about the testbench for this
- a. S should be registers
  - b. S should be wires
  - c. X should be a wire
  - d. Y should be registers
- iv. (2 points) Consider a testbench that replicates the waveform above, after the "initial begin" --- you type
- a. S[1]=0; S[0]=0; X=0;
  - b. #10 S[1]=0; S[0]=1; X=0;
  - c. S[1]=0; S[0]=1; X=0;
  - d. #10 S[1]=0; S[0]=0; X=0;
  - e. S[1]=0; S[0]=0; Y=0;
  - f. #10 S[1]=0; S[0]=0; Y=0;
  - g. #10 S[1]=0; S[0]=1; Y=0;
  - h. S[1]=0; S[0]=1; Y=0;