

1 Boolean Logic Circuits [20 points]

- (a) [10 points] Using Boolean algebra, find the simplest Boolean algebra equation for the following min-terms:
 $\Sigma(1111, 1110, 1000, 1001, 1011, 1010, 0000)$. Show your work step-by-step.

$$F = (\overline{B}.\overline{C}.\overline{D}) + (A.(C + \overline{B}))$$

Explanation:

$$F = (A.B.C.D) + (A.B.C.\overline{D}) + (A.\overline{B}.\overline{C}.\overline{D}) + (A.\overline{B}.\overline{C}.D) + (A.\overline{B}.C.D) + (A.\overline{B}.C.\overline{D}) + (\overline{A}.\overline{B}.\overline{C}.\overline{D})$$

$$F = (\overline{B}.\overline{C}.\overline{D}).(A + \overline{A}) + (A.C).(B.D + B.\overline{D} + \overline{B}.D + \overline{B}.\overline{D}) + (A.\overline{B}).(\overline{C}.D + \overline{C}.\overline{D} + C.D + C.\overline{D})$$

$$F = (\overline{B}.\overline{C}.\overline{D}) + (A.C) + (A.\overline{B})$$

$$F = (\overline{B}.\overline{C}.\overline{D}) + (A.(C + \overline{B}))$$

- (b) [10 points] Convert the following Boolean equation so that it only contains NOR operations. Show your work step-by-step.

$$F = \overline{A} + \overline{(B.C + \overline{A.C})}$$

$$F = \overline{\overline{(\overline{A} + \overline{A} + \overline{(B.C + \overline{A.C})})} + \overline{(\overline{A} + \overline{A} + \overline{(B.C + \overline{A.C})})}}$$

$$B.C = \overline{\overline{B} + \overline{B} + \overline{C} + \overline{C}}$$

$$\overline{A.C} = \overline{\overline{A} + \overline{A} + \overline{C} + \overline{C} + \overline{C} + \overline{C}}$$

Explanation:

$$F = \overline{\overline{(\overline{A} + \overline{(B.C + \overline{A.C})})}}$$

$$F = \overline{\overline{(\overline{A} + \overline{(B.C + \overline{A.C})})} + \overline{(\overline{A} + \overline{(B.C + \overline{A.C})})}}$$

$$F = \overline{\overline{(\overline{A} + \overline{A} + \overline{(B.C + \overline{A.C})})} + \overline{(\overline{A} + \overline{A} + \overline{(B.C + \overline{A.C})})}}$$

$$B.C = \overline{\overline{B} + \overline{B} + \overline{C} + \overline{C}}$$

$$\overline{A.C} = \overline{\overline{A} + \overline{A} + \overline{C} + \overline{C} + \overline{C} + \overline{C}}$$