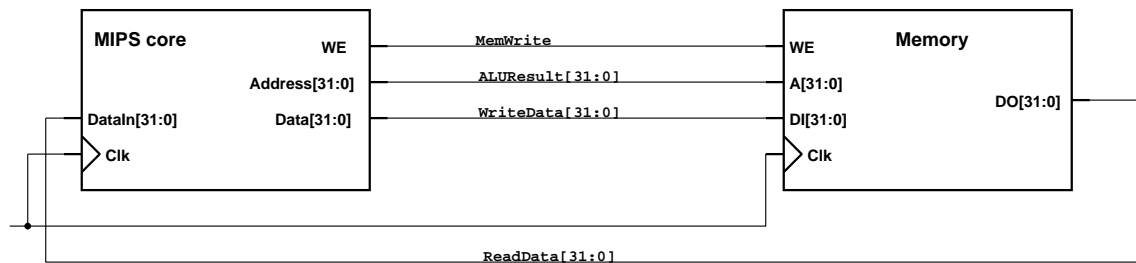


5. (10 points) Seen below is a simplified block diagram of a single-cycle MIPS architecture showing the core to memory interface as covered in the class and lab exercises.



The ADC is connected to the system through a memory mapped interface:

- The MIPS processor can write to Start pin of the ADC.
- The MIPS processor can read the Done pin and the 8-bit DataOut value from the ADC.

The three pins of the ADC are mapped to the following memory addresses:

```
Start    0xFFFF FF00
Done     0xFFFF FF40
DataOut  0xFFFF FF80
```


Make the necessary connections and if necessary add multiplexers, registers, flip-flops so that the processor can read and write to the ADC just as reading/writing to the memory without interfering with the memory. In case you need to compare a value with a memory address, you may use a comparator block that takes two 32-bit inputs and outputs 1 if they match, as shown below.



More specifically, complete the following two functions:

- The input for Start
- The reading of the output for Done and DataOut

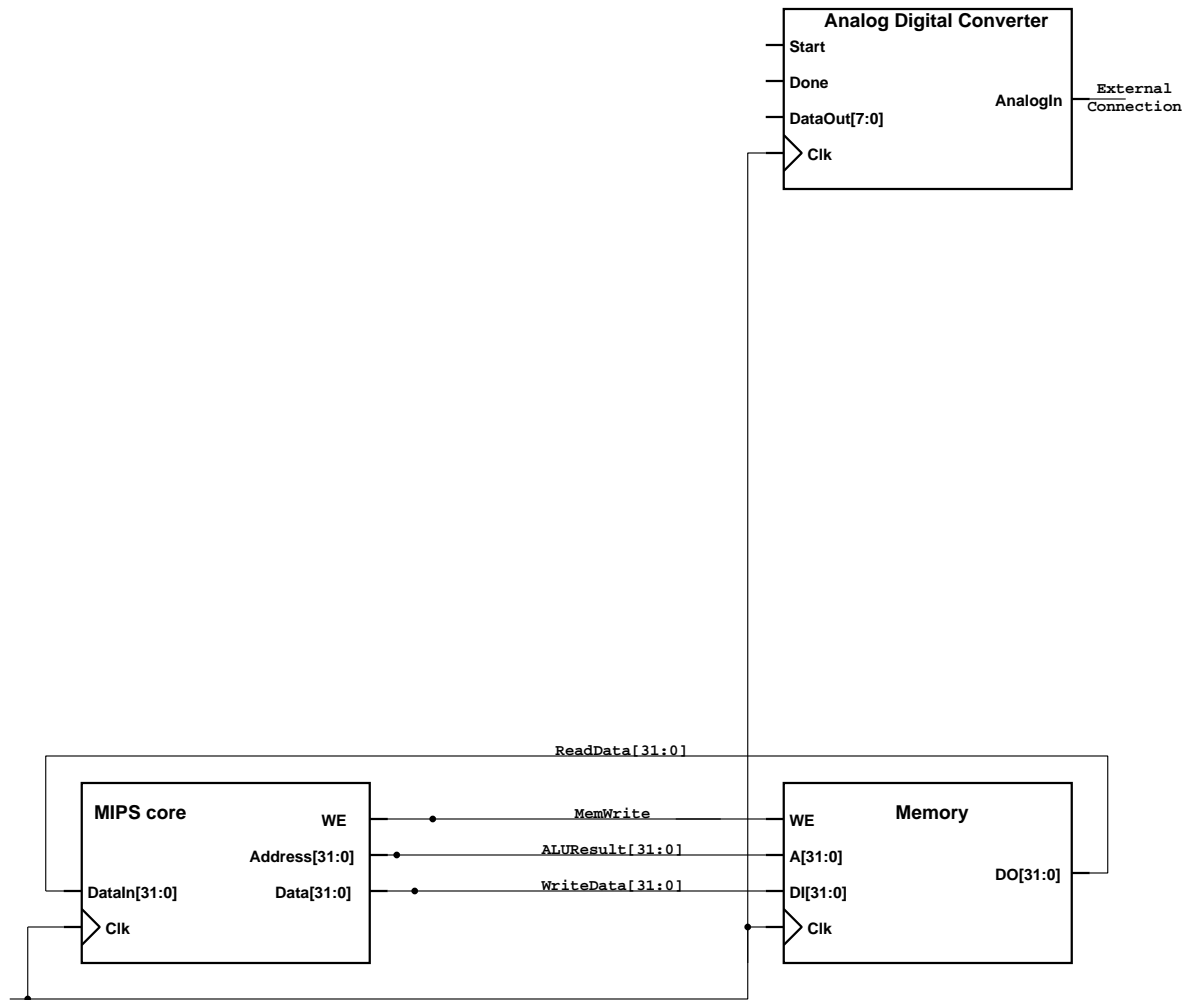Please draw on the schematic on the next page.



Solution:

