

As a member of the Notre Dame community, I acknowledge that it is my responsibility to learn and abide by principles of intellectual honesty and academic integrity, and therefore I will not participate in or tolerate academic dishonesty.

By writing my name below, I agree to uphold the honor code.

Name (print clearly): Siddharth Joshi

**CSE 20221 Logic Design
Midterm Exam, October 07, 2021**

**75 minutes
Closed book, closed notes, no calculator**

Problem	Points	Score
1	10	
2	10	
3	10	
4	10	
5	10	
6	10	
7	10	
8	10	
9	10	
10	10	
Total	100	

Problem 1 (10 points)

- i. (3 points) Let $f = x \& (y \mid (\sim y \mid x) \& z) \mid (y \& \sim z)$. Select all the terms for which the entries of the truth table of f will contain a 1.

- a. $x=0, y=0, z=0$
- b. $x=0, y=0, z=1$
- c. $x=0, y=1, z=0$
- d. $x=0, y=1, z=1$
- e. $x=1, y=0, z=0$
- f. $x=1, y=0, z=1$
- g. $x=1, y=1, z=0$
- h. $x=1, y=1, z=1$

- ii. (2 points) Select which of the following always outputs 0

- a. x^1
- b. x^x
- c. $\sim(x^x)$
- d. x^0

- iii. (5 points) Select all the verilog statements that are equivalent. 1'b1 denotes TRUE and 1'b0 denotes FALSE

- a. `assign f = (x^1'b1)^(y);`
- b. `assign f = (x&y)|~(x|y);`
- c. `assign f = (x^1'b0)^(y);`
- d. `assign f = ~(x&y)|(x|y);`

Problem 2 (10 points)

What are the minimum required number of AND, OR gates required to implement F as a sum-of-products. Assume you have inputs and their complements available as inputs to your circuit.

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- a) One 2-input gate
- b) One 3-input gate
- c) Two 2-input gates
- d) Two 3-input gates
- e) One 2-input gate and one 3-input gate
- f) Three 2-input gates
- g) Three 3-input gates
- h) Two 2-input gates and one 3-input gate
- i) None of the above

Ans : C

Problem 3 (10 points)

Let's use the subscript to denote the base number system. That is: $(1011)_2$ implies binary representation, while $(B)_{16}$ implies the same number in hexadecimal (base-16).

- i. (3 points) Select all the options which are strictly smaller than $(136)_{10}$
 - a. $(1000\ 0100)_2$
 - b. $(89)_{16}$
 - c. $(88)_{16}$
 - d. $(1000\ 1000)_2$
 - e. None of the above

- ii. (5 Points) If all these values are encoded as two's complement, select the true statement:
 - a. $C7 + BB = (7E)_{16}$
 - b. $C7 + BB = (126)_{10}$
 - c. $C7 + BB = (82)_{16}$
 - d. None of the above

- iii. (2 points) If these hexadecimal numbers represent two's complement encoded values, circle the largest value
 - a. C4
 - b. C6
 - c. E8
 - d. 70

Problem 4 (10 points)

(6 points) Each of the numbers below is represented in two's complement, each variable, w, x,y,z can be any hexadecimal value independently of each other.

i.

$$\begin{array}{r} (B3X1)_{16} \\ + (47WZ)_{16} \\ \hline \end{array}$$

- a) i. and ii. both can result in overflow
- b) i. can result in overflow, but not ii.
- c) i. cannot result in overflow but ii. can
- d) neither i. nor ii. can possibly result in an overflow

ii.

$$\begin{array}{r} (7YCD)_{16} \\ + (0110)_{16} \\ \hline \end{array}$$

Ans: C

(4 points) Consider integers $X[15:0]$ and $Y[15:0]$ that result in $SUM[15:0]$ when added. If we know the values of $X[15:14]$ and $Y[15:14]$ as well as $SUM[15]$ we can always determine if there's an overflow:

- a. For signed integers only, not for unsigned integers
- b. For both signed and unsigned integers
- c. For unsigned integers only not for signed integers
- d. We cannot **always** determine if there's been an overflow in either case

Problem 5 (10 points)

1. (3 points) If you had to make a 2:1 multiplexor (2 inputs, 1 select bit) using only NAND gates. How many NAND gates would you need?
 - a. 3
 - b. 4**
 - c. 5
 - d. 6
 - e. 7
 - f. 8
 - g. None of the above

2. (3 points) If you had to make a 2:1 Decoder (2 outputs, 1 select bit) using only NOR gates. How many NOR gates would you need?
 - a. 3
 - b. 4
 - c. 5
 - d. 6
 - e. 7
 - f. 8
 - g. None of the above**

3. (4 points) A Majority gate, with output f and inputs a , b , and c is given by $f = a \& b \mid a \& c \mid b \& c$. If you could only use 2- and 3-input NAND gates, how many such gates would you need to implement this function?
 - a. 3
 - b. 4**
 - c. 5
 - d. 6
 - e. 7
 - f. 8
 - g. None of the above

Problem 6 (10 points)

- i. (2 points) Consider a two-input XOR gate with two inputs and one output. Given the ability to set the inputs to constants (e.g., 1/0). Is it possible to construct a NAND gate using an infinite supply of such two-input XOR gates?

a. Yes

b. No

- ii. (4 points) Given only NAND gates, what is the minimum number of NAND gates needed to implement a two-input XOR.

a. 3

b. 4

c. 5

d. 6

e. 7

f. 8

- iii. (4 points) Below is the Verilog code for two modules, thing and unknown:

```
module thing (  
    input  a,  
    input  b,  
    output y  
);
```

```
    assign y = a & ~b | b & ~a;
```

```
endmodule
```

```
module unknown (  
    input  a,  
    input  b,  
    input  c,
```

```

output y
);

wire w;


thing thing1 (
    .a (a),
    .b (b),
    .y (w)
);

thing thing2 (
    .a (w),
    .b (c),
    .y (y)
);


endmodule

```

 The following waveforms are applied to the inputs of unknown:



 Which of the following is the correct waveform for output y of module unknown?



- a. y1
- b. y2
- c. y3
- d. y4

Problem 7 (10 points)

i. (3 points) Given a Karnaugh map for a 4-input function, the maximum number of product terms that can ever remain after minimization are:

a. 6

b. 7

c. 8

d. 9

e. Impossible to determine without knowing the entries

ii. (3 points) Select all the correctly minimized expressions for the K-Map below

ab \ cd	00	01	11	10
00		1	1	1
01				
11				
10	1			1


a. $(\sim a \& \sim b \& d) \mid (a \& \sim b \& \sim d) \mid (\sim a \& \sim b \& c)$

b. $(\sim a \& \sim b \& d) \mid (a \& \sim b \& \sim d) \mid (\sim b \& c \& \sim d)$

c. $(\sim a \& \sim b \& d) \mid (a \& \sim b \& \sim d) \mid (\sim b \& c \& \sim d) \mid (\sim a \& \sim b \& c)$

d. none of the above

 
iii. (4 points) Correctly fill out the truth table for the given circuit.



A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

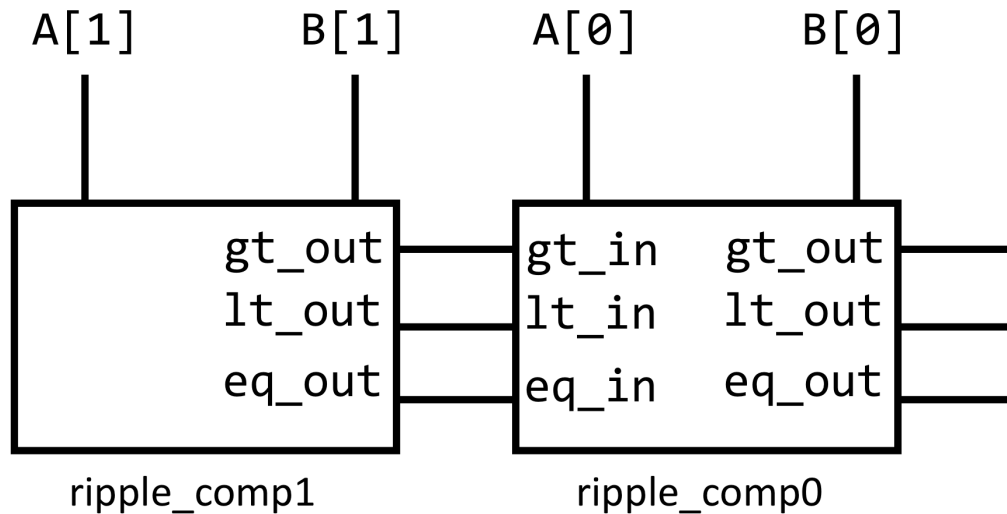Problem 8 (10 points)

A ripple comparator, like a ripple carry adder, chains instances of a single comparator module to output whether one unsigned integer is larger than, equal to, or lesser than the other. In this problem we will design such a comparator for two bit values. Note, that unlike in a ripple carry adder, for the comparator the comparison should start at the MSB and end at the LSB.



- i. (3 points) Complete the verilog module for `ripple_comp1`. To get you started, if `A[1] = 1` and `B[1] = 0`; `gt_out = 1`;
- ```
module ripple_comp1(
 input a,
 input b,
 output eq_out,
 output gt_out,
 output lt
);
 assign gt_out = a&~b;
 assign lt_out = ~a&b;
 assign eq_out = ~(a^b);

endmodule
```

- ii. (3 points) Complete the truth table for ripple\_comp0. X indicates that the value doesn't matter. e.g. if gt\_in = 1, then the value of the LSBs don't matter.

| A[0] | B[0] | gt_in | lt_in | eq_in | gt_out | lt_out | eq_out |
|------|------|-------|-------|-------|--------|--------|--------|
| x    | x    | 1     | x     | x     | 1      | 0      | 0      |
| x    | x    | x     | 1     | x     | 0      | 1      | 0      |
| 0    | 0    | x     | x     | 1     | 0      | 0      | 1      |
| 0    | 1    | x     | x     | 1     | 0      | 1      | 0      |
| 1    | 0    | x     | x     | 1     | 1      | 0      | 0      |
| 1    | 1    | x     | x     | 1     | 0      | 0      | 1      |

- iii. (4 points) complete the verilog code for ripple\_comp0

```
module ripple_comp0(
input a,
input b,
input gt_in,
input eq_in,
input lt_in,
output eq_out,
output gt_out,
output lt
);

assign gt_out = gt_in | (a&~b) ; //students could also & the second term with eq_in
assign lt_out = lt_in | (~a&b) ;
assign eq_out = eq_in | ~(a^b) ;

endmodule
```

### Problem 9 (10 points)

A De-Multiplexor or a DEMUX takes an input (X) and places it on one of  $2^n$  outputs ( $Y[2^n-1:0]$ ) based on an n-bit selection input ( $S[n-1:0]$ ).



- i. (4 points) Complete the verilog code below to correctly describe a DEMUX.

```
module demux(
 input X,
 input S,
 output [1:0] Y
);
```

```
 assign Y[0] = X&~S;
 assign Y[1] = X&S;
```

```
endmodule
```

  - ii. (2 points) Fill in the timing diagram, with the correct waveforms for  $Y[3:0]$



Answer some questions about a testbench for the DEMUX.

iii. (2 points) Select all the true statements about the testbench for this

- a. S should be registers**
- b. S should be wires
- c. X should be a register**
- d. X should be a wire
- e. Y should be registers
- f. **Y should be wires**

iv. (2 points) Consider a testbench that replicates the waveform above, after the "initial begin" --- you type

- a. S[1]=0; S[0]=0; X=0;
- b. #10 S[1]=0; S[0]=1; X=0;
- c. S[1]=0; S[0]=1; X=0;**
- d. #10 S[1]=0; S[0]=0; X=0;
- e. S[1]=0; S[0]=0; Y=0;
- f. #10 S[1]=0; S[0]=0; Y=0;
- g. #10 S[1]=0; S[0]=1; Y=0;
- h. S[1]=0; S[0]=1; Y=0;

### Problem 10 (10 points)

The following represents machine code to be implemented on Albacore. This code is meant to loop a few times and then terminate.

| Addr | Label | Pseudocode | Assembly | Hex  |
|------|-------|------------|----------|------|
| 0    |       |            |          | 7000 |
| 1    |       |            |          | 7101 |
| 2    |       |            |          | 7222 |
| 3    |       |            |          | 3312 |
| 4    |       |            |          | B033 |
| 5    |       |            |          | 0001 |
| 6    |       |            |          | 6331 |
| 7    |       |            |          | AFD0 |
| 8    |       |            |          | F000 |

i. (3 Points) As currently written, this code results in an infinite loop. If this error can be fixed by changing just a single line, circle the line number corresponding to the line number which has the error.

0    1    2    3    4    5    6    7    8

ii. (4 Points) Write down the **assembly** code for the corrected command below

BZ, R3, 4

iii. (3 points) What is the value of R0 after the corrected program is executed.

- a. 0x0005
- b. 0x0006**
- c. 0x0007
- d. 0x0008



## albaCore Instruction Set and Encoding

| Assembly Language Syntax |          |      |         | Behavior                                                                                              |
|--------------------------|----------|------|---------|-------------------------------------------------------------------------------------------------------|
| add                      | rw       | ra   | rb      | $R[ra] \leftarrow R[ra] + R[rb]$                                                                      |
| sub                      | rw       | ra   | rb      | $R[ra] \leftarrow R[ra] - R[rb]$                                                                      |
| and                      | rw       | ra   | rb      | $R[ra] \leftarrow R[ra] \& R[rb]$                                                                     |
| or                       | rw       | ra   | rb      | $R[ra] \leftarrow R[ra]   R[rb]$                                                                      |
| not                      | rw       | ra   |         | $R[ra] \leftarrow \sim R[ra]$                                                                         |
| shl                      | rw       | ra   | shamt4  | $R[ra] \leftarrow R[ra] \ll \text{shamt4}$                                                            |
| shr                      | rw       | ra   | shamt4  | $R[ra] \leftarrow R[ra] \gg \text{shamt4}$                                                            |
| ldi                      | rw       | imm8 |         | $R[ra] \leftarrow \{4'h0, \text{imm8}\}$                                                              |
| ld                       | rw       | rb   | offset4 | $R[ra] \leftarrow M[R[rb] + \text{offset4}]$                                                          |
| st                       | ra       | rb   | offset4 | $M[R[rb] + \text{offset4}] \leftarrow R[ra]$                                                          |
| br                       | disp8    |      |         | $pc \leftarrow pc + \text{signExtend}(\text{disp8})$                                                  |
| bz                       | rb       | disp |         | if $(R[rb] == 0)$ $pc \leftarrow pc + \text{signExtend}(\text{disp8})$<br>else $pc \leftarrow pc + 1$ |
| bn                       | rb       | disp |         | if $(R[rb] < 0)$ $pc \leftarrow pc + \text{signExtend}(\text{disp8})$<br>else $pc \leftarrow pc + 1$  |
| jal                      | target12 |      |         | $pc \leftarrow \{pc[15:12, \text{target12}]\}$<br>$R[15] \leftarrow pc + 1$                           |
| jr                       | ra       |      |         | $pc \leftarrow R[ra]$                                                                                 |
| quit                     |          |      |         | pc freezes                                                                                            |

| Instruction |        |      |           | Encoding    |    |    |    |              |    |   |   |           |   |   |   |       |   |   |   |
|-------------|--------|------|-----------|-------------|----|----|----|--------------|----|---|---|-----------|---|---|---|-------|---|---|---|
| mnemonic    | arg1   | arg2 | arg3      | 15          | 14 | 13 | 12 | 11           | 10 | 9 | 8 | 7         | 6 | 5 | 4 | 3     | 2 | 1 | 0 |
| add         | rw     | ra   | rb        | opcode = 0  |    |    |    | rw           |    |   |   | ra        |   |   |   | rb    |   |   |   |
| sub         | rw     | ra   | rb        | opcode = 1  |    |    |    | rw           |    |   |   | ra        |   |   |   | rb    |   |   |   |
| and         | rw     | ra   | rb        | opcode = 2  |    |    |    | rw           |    |   |   | ra        |   |   |   | rb    |   |   |   |
| or          | rw     | ra   | rb        | opcode = 3  |    |    |    | rw           |    |   |   | ra        |   |   |   | rb    |   |   |   |
| not         | rw     | ra   |           | opcode = 4  |    |    |    | rw           |    |   |   | ra        |   |   |   |       |   |   |   |
| shl         | rw     | ra   | shamt     | opcode = 5  |    |    |    | rw           |    |   |   | ra        |   |   |   | shamt |   |   |   |
| shr         | rw     | ra   | shamt     | opcode = 6  |    |    |    | rw           |    |   |   | ra        |   |   |   | shamt |   |   |   |
| ldi         | rw     | imm  |           | opcode = 7  |    |    |    | rw           |    |   |   | imm       |   |   |   |       |   |   |   |
| ld          | rw     | rb   | offset_ld | opcode = 8  |    |    |    | rw           |    |   |   | offset_ld |   |   |   | rb    |   |   |   |
| st          | ra     | rb   | offset_st | opcode = 9  |    |    |    | offset_st    |    |   |   | ra        |   |   |   | rb    |   |   |   |
| br          | disp   |      |           | opcode = 10 |    |    |    | displacement |    |   |   |           |   |   |   |       |   |   |   |
| bz          | rb     | disp |           | opcode = 11 |    |    |    | displacement |    |   |   |           |   |   |   | rb    |   |   |   |
| bn          | rb     | disp |           | opcode = 12 |    |    |    | displacement |    |   |   |           |   |   |   | rb    |   |   |   |
| jal         | target |      |           | opcode = 13 |    |    |    | target       |    |   |   |           |   |   |   |       |   |   |   |
| jr          | ra     |      |           | opcode = 14 |    |    |    |              |    |   |   | ra        |   |   |   |       |   |   |   |
| quit        |        |      |           | opcode = 15 |    |    |    |              |    |   |   | imm       |   |   |   |       |   |   |   |