

3 Boolean Algebra [15 points]

- (a) [5 points] Find the simplest sum-of-products representation of the following Boolean equation. Show your work step-by-step.

$$F = B + (A + \overline{C}).(\overline{A} + \overline{B} + \overline{C})$$

Answer: $F = A + B + \overline{C}$

Explanation:

$$F = B + (A.\overline{A} + A.\overline{B} + A.\overline{C} + \overline{A}.\overline{C} + \overline{B}.\overline{C} + \overline{C}.\overline{C})$$

$$F = B + 0 + A.\overline{B} + \overline{C}.(A + \overline{A}) + \overline{B}.\overline{C} + \overline{C}$$

$$F = (B + A.\overline{B}) + \overline{C}.(A + \overline{A}) + (\overline{B}.\overline{C} + \overline{C})$$

$$F = (B + A) + \overline{C} + \overline{C}.(B + 1)$$

$$F = A + B + \overline{C}$$

- (b) [5 points] Convert the following Boolean equation so that it only contains NAND operations. Show your work step-by-step.

$$F = \overline{(A + B.C)} + \overline{C}$$

Answer: $F = \overline{\overline{\overline{(A.A)}.(B.C))}.C$

Explanation:

$$F = \overline{\overline{\overline{(A + B.C)} + \overline{C}}}$$

$$F = \overline{\overline{(A + B.C).C}}$$

$$F = \overline{\overline{(A + B.C).C}}$$

$$F = \overline{\overline{(\overline{A}.\overline{(B.C))}.C}}$$

$$F = \overline{\overline{((A.A).(B.C)).C}}$$

- (c) [5 points] Using Boolean algebra, simplify the following min-terms: $\sum(3, 5, 7, 11, 13, 15)$
Show your work step-by-step.

Answer: $F = D.(B + C)$

Explanation:

$$\{3, 5, 7, 11, 13, 15\} = \{0011, 0101, 0111, 1011, 1101, 1111\}$$

$$F = (\overline{A}.\overline{B}.C.D) + (\overline{A}.B.\overline{C}.D) + (\overline{A}.B.C.D) + (A.\overline{B}.C.D) + (A.B.\overline{C}.D) + (A.B.C.D)$$

$$F = (C.D.((\overline{A}.\overline{B}) + (\overline{A}.B) + (A.\overline{B}) + (A.B))) + (B.D.((\overline{A}.\overline{C}) + (A.\overline{C})))$$


$$F = (C.D) + (B.\overline{C}.D)$$

$$F = D.(C + (B.\overline{C}))$$

$$F = D.(B + C)$$

4 Finite State Machine [50 points]

You are given the following FSM with two one-bit input signals (T_A and T_B) and one two-bit output signal (O). You need to implement this FSM, but you are unsure about how you should encode the states. Answer the following questions to get a better sense of the FSM and how the three different types of state encoding we discussed in the lecture (i.e., one-hot, binary, output) will affect the implementation.

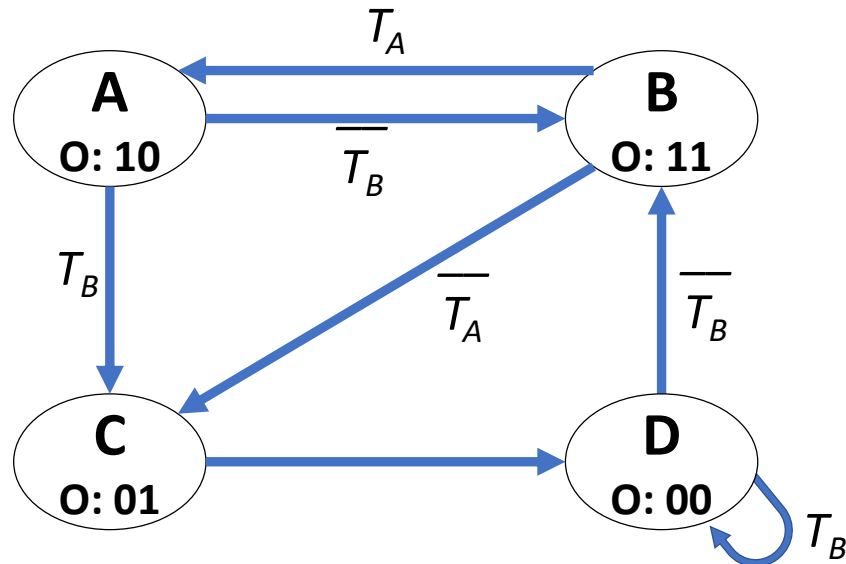

- (a) [3 points] There is one critical component of an FSM that is *missing* in this diagram. Please write what is missing in the answer box below.

The reset line or indication for initial state.

- (b) [2 points] Of the two FSM types, what type of an FSM is this?

Moore

(c) [5 points] List one major advantage of each type of state encoding below.

One-hot encoding	reduces next-state logic
------------------	--------------------------

Binary encoding	reduces FFs to hold state
-----------------	---------------------------

Output encoding	reduces the output logic
-----------------	--------------------------

(d) [10 points] Fully describe the FSM with equations given that the states are encoded with **one-hot** encoding. Assign state encodings such that numerical values of states increase monotonically for states A through D while using the **minimum** possible number of bits to represent the states with one-hot encoding. Indicate the values you assign to each state *and* simplify all equations:

State assignments: A: 0001, B: 0010, C: 0100, D: 1000

$$NS[3] = TB * TS[3] + TS[2]$$

$$NS[2] = TB * TS[0] + \overline{TA} * TS[1]$$

$$NS[1] = \overline{TB} * (TS[0] + TS[3])$$

$$NS[0] = TS[1] * TA$$

$$O[1] = TS[0] + TS[1]$$

$$O[0] = TS[1] + TS[2]$$

- (e) [10 points] Fully describe the FSM with equations given that the states are encoded with **binary** encoding. Assign state encodings such that numerical values of states increase monotonically for states A through D while using the **minimum** possible number of bits to represent the states with binary encoding. Indicate the values you assign to each state *and* simplify all equations:

State assignments: A: 00, B: 01, C: 10, D: 11

$$NS[1] = \overline{TS[1]} * (\overline{TS[0]} * TB + TS[0] \overline{TA}) + TS[1] * (\overline{TS[0]} + TS[0] * TB)$$

$$NS[0] = \overline{TS[1]} * \overline{TS[0]} * \overline{TB} + TS[1]$$

$$O[1] = TS[1]$$

$$O[0] = TS[1] \text{ XOR } TS[0]$$

- (f) [10 points] Fully describe the FSM with equations given that the states are encoded with **output** encoding. Use the **minimum** possible number of bits to represent the states with output encoding. Indicate the values you assign to each state *and* simplify all equations:

State assignments: A: 10, B: 11, C: 01, D: 00

$$NS[1] = TS[1] * \overline{TS[0]} * \overline{TB} + TS[1] * TS[0] * TA + \overline{TS[1]} * \overline{TS[0]} * \overline{TB}$$

$$= \overline{TS[0]} * \overline{TB} + TS[1] * TS[0] * TA$$

$$NS[0] = TS[1] * \overline{TS[0]} + TS[1] * TS[0] * \overline{TA} + \overline{TS[1]} * \overline{TS[0]} * \overline{TB}$$

$$= TS[1] * (\overline{TS[0]} + TS[0] * \overline{TA}) + \overline{TS[1]} * \overline{TS[0]} * \overline{TB}$$

$$O[1] = TS[1]$$

$$O[0] = TS[0]$$