 


Draw a proper state transition diagram that corresponds to the FSM described in this Verilog code.

(25 points should be given only if the diagram is absolutely correct)



- (c) [5 points] Is the FSM described by the previous Verilog code a Moore or a Mealy FSM? Why?

Moore, the output Z only depends on the state (*presentState*) and not on the input (A).

3 Verilog

Please answer the following four questions about Verilog.

- (a) [10 points] Does the following code result in a sequential circuit or a combinational circuit? Please explain why.

```
1 module one (input clk, input a, input b, output reg [1:0] q);
2   always @ (*)
3     if (b)
4       q <= 2'b01;
5     else if (a)
6       q <= 2'b10;
7 endmodule
```

Answer and concise explanation:

This code results in a sequential circuit because a latch is required to store the old value of `q` if both conditions are **not** satisfied.

- (b) [10 points] What is the value of the output `z` if the input `c` is 10101111 and `d` is 01010101?

```
1 module two (input [7:0] c, input [7:0] d, output reg [7:0] z);
2   always @ (c,d)
3     begin
4       z = 8'b00000001;
5       z[7:5] = c[5:3];
6       z[4] = d[7];
7       z[3] = d[7];
8     end
9 endmodule
```

Please answer below. Show your work.

10100001. Last assignment of a bit overrides all previous assignments.