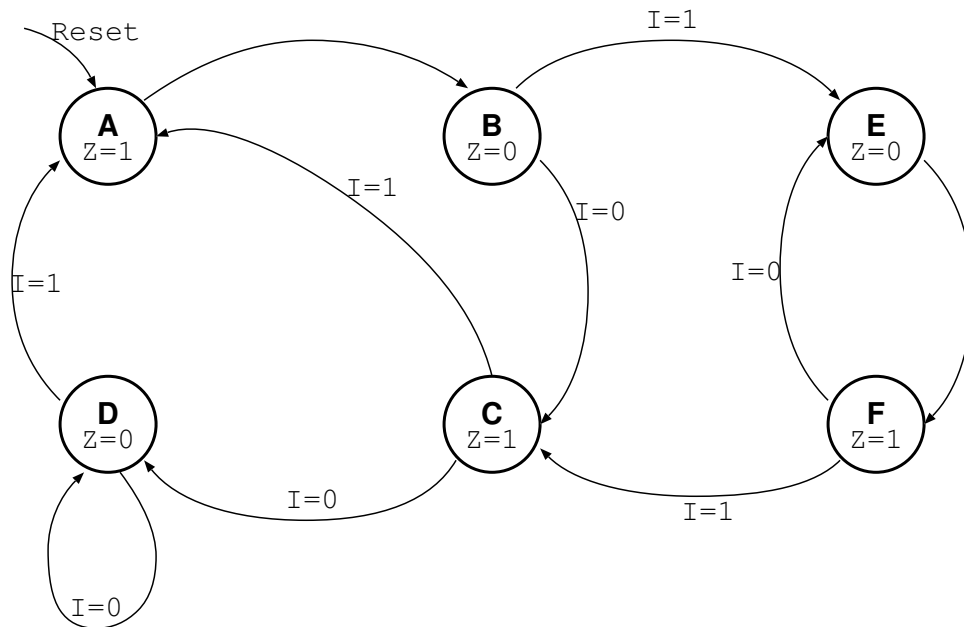


2. Consider the following state diagram of an FSM with 1-bit input ( $I$ ) and 1-bit output ( $Z$ ).



The state has been coded using a 3-bit vector  $S = S_2 S_1 S_0$  according to the following table:

State			
name	$S_2$	$S_1$	$S_0$
A	0	0	0
B	0	0	1
C	0	1	0
D	0	1	1
E	1	0	0
F	1	0	1

- (a) (1 point) Is this a Moore or Mealy type FSM? Briefly explain.

**Solution:** Moore, outputs depend only on the present state and nothing else.

- (b) (6 points) Fill in the following state transition table that determines the next state vector  $N = N_2 N_1 N_0$  based on the current state  $S$  and the input  $I$ .

State				Input	Next State			
name	$S_2$	$S_1$	$S_0$	$I$	name	$N_2$	$N_1$	$N_0$
A	0	0	0	X	B	0	0	1
B	0	0	1	0	C	0	1	0
B	0	0	1	1	E	1	0	0
C	0	1	0	0	D	0	1	1
C	0	1	0	1	A	0	0	0
D	0	1	1	0	D	0	1	1
D	0	1	1	1	A	0	0	0
E	1	0	0	X	F	1	0	1
F	1	0	1	0	E	1	0	0
F	1	0	1	1	C	0	1	0

*Note that there are different ways of writing this table to represent the same result.*

- (c) (3 points) Write the Next State Equations from the table you have filled above using either *Product of Sums (POS)* or *Sum of Products (SOP)* form. **Do not spend time minimizing the equations, this will be next question.**

**Solution:**

$$N_0 = \overline{S_2} \overline{S_1} \overline{S_0} + \overline{S_2} S_1 \overline{S_0} \overline{I} + \overline{S_2} S_1 S_0 \overline{I} + S_2 \overline{S_1} \overline{S_0}$$

$$N_1 = \overline{S_2} \overline{S_1} S_0 \overline{I} + \overline{S_2} S_1 \overline{S_0} \overline{I} + \overline{S_2} S_1 S_0 \overline{I} + S_2 \overline{S_1} S_0 I$$

$$N_2 = \overline{S_2} \overline{S_1} S_0 I + S_2 \overline{S_1} \overline{S_0} + S_2 \overline{S_1} S_0 \overline{I}$$

- (d) (6 points) Minimize the Next State Equations from the previous part. Note that the FSM requires only six states. This means that there are several State ( $S$ ) / Input( $I$ ) combinations for which the outputs can be treated as *Don't Care*, which should help minimizing the boolean equations.

*Hint: Consider using Karnaugh diagrams to solve this problem.*

**Solution:**

It is important to note that for  $S_2 S_1 = 11$  the next state  $N$  can be taken as  $N_2 N_1 N_0 = XXX$ . This can simplify the Boolean equations significantly. It is best to use a Karnaugh map to find the simplifications.

$\begin{array}{c} S_0 I \\ \hline S_2 S_1 \end{array}$		$S_0 I$			
		00	01	11	10
00	00	1	1	0	0
	01	1	0	0	1
11	11	X	X	X	X
	10	1	1	0	0

**$N_0$**

$\begin{array}{c} S_0 I \\ \hline S_2 S_1 \end{array}$		$S_0 I$			
		00	01	11	10
00	00	0	0	0	1
	01	1	0	0	1
11	11	X	X	X	X
	10	0	0	1	0

**$N_1$**

$\begin{array}{c} S_0 I \\ \hline S_2 S_1 \end{array}$		$S_0 I$			
		00	01	11	10
00	00	0	0	1	0
	01	0	0	0	0
11	11	X	X	X	X
	10	1	1	0	1

**$N_2$**

$$N_0 = \overline{S_1} \overline{S_0} + S_1 \overline{I}$$

$$N_1 = S_1 \overline{I} + S_2 S_0 I + \overline{S_2} S_0 \overline{I}$$

$$N_2 = S_2 \overline{S_0} + S_2 \overline{I} + \overline{S_2} \overline{S_1} S_0 I$$