

4. (10 points) There are four Verilog code snippets in this section. For each code, first state whether or not there is a mistake. If there is a mistake explain how to correct it.
Note: Assume that the behavior as described, is correct

(a)

```

1 module mux2 ( input [1:0] i, output s, input z);
2     assign s= (z) ? i[1]:i[0];
3 endmodule
4
5 module one (input [3:0] data, input sel1, input sel2, output z );
6     wire [1:0] temp ;
7
8     mux2 i0 (data[1:0], sel1, temp[0]);
9     mux2 i1 (data[3:2], sel1, temp[1]);
10    mux2 final (temp, sel2, z);
11 endmodule

```

Solution: This code is not correct. It uses an ordered instantiation template where the ordering of the pins should correspond to the order they are declared. This itself is not wrong, but the *input* signals on the second position (sel1,sel2) connect to the *output* of the instance *mux*. Either the ordering of *mux2* needs to be changed, or the ordering of the elements the instantiation. The better option would be to use a *connect by name*.

(b)

```

1 module two (input [3:0] a, input [0:3] b, output reg [3:0] z);
2     always @ ( *)
3         if (a == 0)
4             z={b[0],b[1],b[2],b[3]};
5         else
6             z=a+b;
7 endmodule

```

Solution:

The code is syntactically correct. There is a lot of unnecessary code: using one input as [0:3] and the other as [3:0] is not the smartest choice, the entire code could be written as *assign z=a+b*, but syntactically the code is correct.

(c)

```

1 module three (clk, rst, a, b, c, z);
2   input a,b,c,clk,rst;
3   output reg z;
4   reg q;
5
6   always @ (*)
7     begin
8       q <= a ^ b;
9       if (c) q <= ~(a^b);
10    end
11  always @ (negedge clk)
12    if (rst) z= 1'b0;
13    else    z= q;
14 endmodule

```

Solution: The code is syntactically correct. Once again, it is a bit unconventional. One always block use blocking statements and the other non-blocking statements. Both would work, although it would probably be more efficient to write them otherwise.

(d)

```

1 module four (input [2:0] sel, output reg [5:0] z);
2   case (sel)
3     0: z = 6'b00_0000;
4     1: z = 6'b00_0001;
5     2: z = 6'b00_0011;
6     3: z = 6'b00_0111;
7     4: z = 6'b00_1111;
8     5: z = 6'b01_1111;
9     6: z = 6'b11_1111;
10    default: z= 6'b00_0000;
11  endcase
12 endmodule

```

Solution: This code is not correct. The case statement is a sequential statement that needs to be within an always statement.